

Simulated RLC Time Response (10k Ω)

