

**Simulated RLC Time Response ( $680\Omega$ )**

